

ENGR 3020 Home Assignment 2

100 Points


Name: arianna banton

NOTE: SHOW ALL YOUR WORK. WRITING THE ANSWERS WITHOUT SHOWING YOUR WORK WILL RESULT IN NO POINTS.

Chp4.

4. Determine the resistance between pins 2 and 3 in the circuit board in [Figure 4–65](#).

Figure 4–65

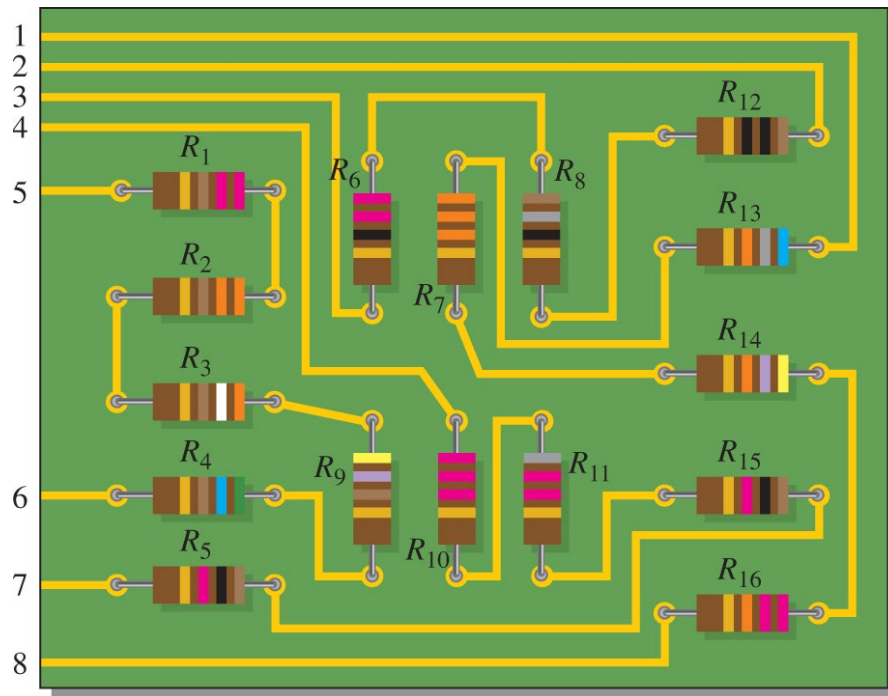

11. Determine the resistance between each of the following sets of pins on the PC board in [Figure 4–65](#).


- | | |
|--------------------|------|
| a. pin 1 and pin 8 | a. 4 |
| b. pin 2 and pin 3 | b. 3 |
| c. pin 4 and pin 7 | c. 4 |
| d. pin 5 and pin 6 | d. 5 |

15. What is the current in each circuit of [Figure 4-70](#)? Show how to connect an ammeter in each case.


The first circuit diagram shows a 5.5-volt voltage source whose positive and negative terminals are connected across a vertical branch that consists of three resistors R_1 , R_2 , and R_3 with values as 2.2 kilo ohms, 5.6 kilo ohms, and 1 kilo ohm respectively.

The second circuit diagram shows three branches in series arranged in the form of a right triangle. The vertical branch consists a 16-volt voltage supply whose positive terminal is connected to resistor R_1 with value as 1 mega ohm. The negative terminal is connected to resistor R_3 with value as 560 kilo ohms. The diagonal branch has a resistor R_2 with value as 2.2 mega ohms.

Figure 4-70

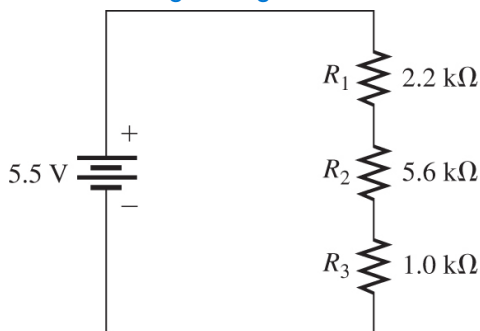

(a)

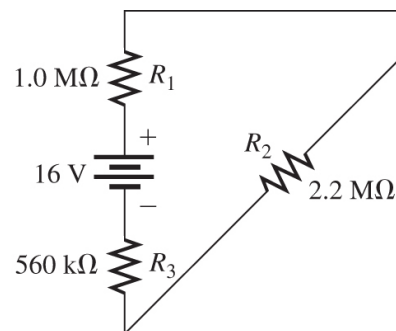

(b)

to connect an ammeter: place the ammeter in series with each resistor to measure the current flowing through each resistor.

15-16

b. $r_1 = 1000000$

$r_2 = 2200000$

$r_3 = 560000$

total resistance:

$1000000 + 2200000 + 560000 = 3760000$

total current: $16 / 3760000 = .00000426A$

voltage:

$r_1 = .0$

$0000426A * 1000000 = 4.26$


$r_2 = .00000426A * 2200000 = 9.372$

$r_3 = .00000426A * 560000 = 2.3856$


16. Determine the voltage across each resistor in [Figure 4-70](#).

23. Determine the unspecified voltage drop(s) in each circuit of [Figure 4-71](#). Show how to connect a voltmeter to measure each unknown voltage drop.

Figure 4-71

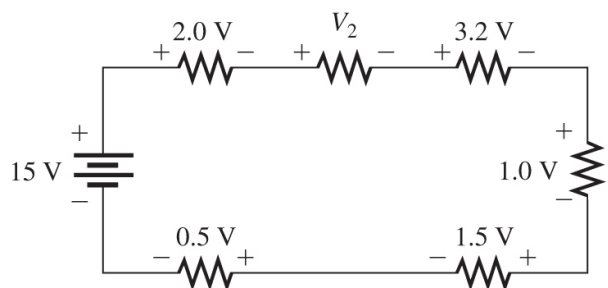

(a)

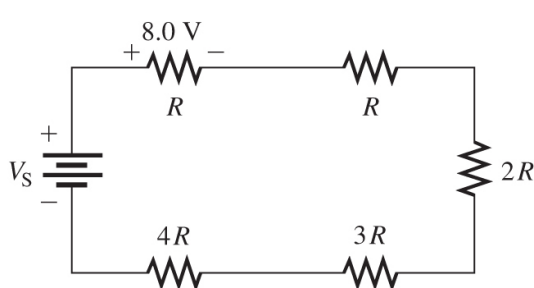


(b)

$$\begin{aligned} a. & 2.0V + 3.2V + 1V + 1.5V + .5V = 8.2 \\ & 15 - 8.2 = 6.8V \\ & V_2 = 6.8V \end{aligned}$$


$$\begin{aligned} b. & 8 = V_s \times (R / R + R + 2R + 3R + 4R) \\ & 8 = V_s \times (R / 11R) \\ & 8 = V_s \times (1 / 11) \\ & V_s = 88V \end{aligned}$$

31. Find the total power in [Figure 4–75](#).

Figure 4–75

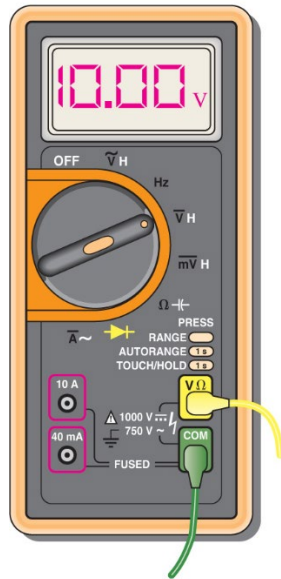


(a) Meter with leads going to protoboard

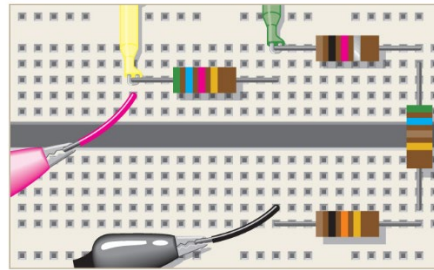

(b) Protoboard with meter leads (yellow and green) and power supply leads (red and black) connected

voltage = 10V
current = 10A
power = $10V \times 10A = 100 \text{ ohms}$

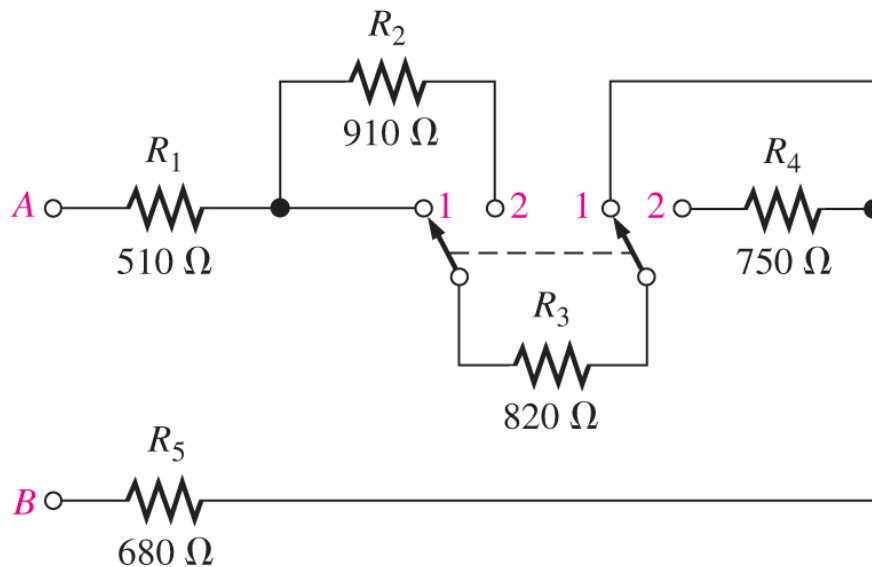50. What is the total resistance from A to B for each switch position in Figure 4–84?



$$510 + 820 + 680 = 2010 \text{ ohms}$$